



LECTURE NOTES

ON

Digital Electronics

Prepared by

Pampa Nandi

(Assistant Professor in Department of Electronics and Telecommunication Engineering, KIIT Polytechnic BBSR)

Email : pmandifet@kp.kiit.ac.in

CONTENTS

Sl.No	Chapter Name	Page No
1	Basics of Digital Electronics	3-17
2	Combinational logic circuits	18-24
3	Sequential logic Circuits	25-30
4	Registers, Memories & PLD	31-34
5	A/D and D/A Converters	35-37
6	LOGIC FAMILIES	38-41

Unit-1: Basics of Digital Electronics

A Digital system is an interconnection of digital modules and it is a system that manipulates discrete elements of information that is represented internally in the binary form. Now a day's digital systems are used in wide variety of industrial and consumer products such as automated industrial machinery, pocket calculators, microprocessors, digital computers, digital watches, TV games and signal processing and so on.

Number System-Binary, Octal, Decimal, Hexadecimal - Conversion from one system to another number system.

Number :

The way of quantifying anything , represented through various combination of symbols is called number.

Digit :

The various symbols representing a single number in any number system is called digit. E.g. Decimal number system (Arabic numerals): Digits: 0,1,2,3,4,5,6,7,8,9.

Radix / Base (r) :

The maximum number of different digits of any number system. E.g Decimal NS, $r = 10$

Number system:

The properly structured number formation is called Number system. In number system there are different symbols and each symbol has an absolute value and also has place value.

In general a number in a system having base or radix ' r ' can be written as

Number various combination digits according to position

$N_r = [\text{Integer part} . \text{Fractional part}]$

↑ Radix point

$$= d_n d_{n-1} \dots d_1 d_0 . d_{-1} d_{-2} \dots d_{-m}$$

The value,

$$N_{10} = d_n \times r^n + d_{n-1} \times r^{n-1} + \dots + d_1 \times r^1 + d_0 \times r^0 + d_{-1} \times r^{-1} + d_{-2} \times r^{-2} + \dots + d_{-m} \times r^{-m}$$

* The right most digit of any number is called Least Significant Digit

* The left most digit of any number is called Most Significant Digit

TYPES OF NUMBER SYSTEM:-

There are four types of number systems. They are

1. Decimal number system
2. Binary number system
3. Octal number system
4. Hexadecimal number system

DECIMAL NUMBER SYSTEM:- •

The decimal number system contain ten unique symbols 0,1,2,3,4,5,6,7,8 and 9.

- In decimal system 10 symbols are involved, so the base or radix is 10.
- It is a positional weighted system.

$$(d_n \times 10^n) + (d_{n-1} \times 10^{n-1}) + (d_{n-2} \times 10^{n-2}) + \dots + (d_0 \times 10^0) + (d_{-1} \times 10^{-1}) + (d_{-2} \times 10^{-2}) + \dots + (d_{-m} \times 10^{-m})$$

For example:-

$$\begin{aligned} 9256.26 &= 9 \times 1000 + 2 \times 100 + 5 \times 10 + 6 \times 1 + 2 \times (1/10) + 6 \times (1/100) \\ &= 9 \times 10^3 + 2 \times 10^2 + 5 \times 10^1 + 6 \times 10^0 + 2 \times 10^{-1} + 6 \times 10^{-2} \end{aligned}$$

BINARY NUMBER SYSTEM:-

- The binary number system is a positional weighted system.
- The base or radix of this number system is 2.
- It has two independent symbols, The symbols used are 0 and 1.
- A binary digit is called a bit

$$(d_n \times 2^n) + (d_{n-1} \times 2^{n-1}) + (d_{n-2} \times 2^{n-2}) + \dots + (d_0 \times 2^0) + (d_{-1} \times 2^{-1}) + (d_{-2} \times 2^{-2}) + \dots + (d_{-k} \times 2^{-k})$$

OCTAL NUMBER SYSTEM:-

- It is also a positional weighted system.
- Its base or radix is 8.
- It has 8 independent symbols 0,1,2,3,4,5,6 and 7.
- Its base $8 = 2^3$, every 3-bit group of binary can be represented by an octal digit.

HEXADECIMAL NUMBER SYSTEM:-

- The hexadecimal number system is a positional weighted system.
- The base or radix of this number system is 16.
- The symbols used are 0,1,2,3,4,5,6,7,8,9,A,B,C,D,E and F
- The base $16 = 2^4$, every 4-bit group of binary can be represented by an hexadecimal digit.

CONVERSION FROM ONE NUMBER SYSTEM TO ANOTHER :-

1. BINARY NUMBER SYSTEM:-

(a) Binary to decimal conversion:- In this method, each binary digit of the number is multiplied by its positional weight and the product terms are added to obtain decimal number.

$$\begin{aligned}
 (111.101)_2 &= (1 \times 2^2) + (1 \times 2^1) + (1 \times 2^0) + (1 \times 2^{-1}) + (0 \times 2^{-2}) + (1 \times 2^{-3}) \\
 &= 4 + 2 + 1 + 0.5 + 0 + 0.125 \\
 &= (7.625)_{10}
 \end{aligned}$$

(b) Binary to Octal conversion:- For conversion binary to octal the binary numbers are divided into groups of 3 bits each, starting at the binary point and proceeding towards left and right.

(i) Convert $(101111010110.110110011)_2$ into octal.

Solution :

Group of 3 bits are	101	111	010	110	.	110	110	011
Convert each group into octal =	5	7	2	6	.	6	6	3

The result is **$(5726.663)_8$**

(c) Binary to Hexadecimal conversion:- For conversion binary to hexadecimal number the binary numbers starting from the binary point, groups are made of 4 bits each, on either side of the binary point.

(ii) Convert $(01011111011.011111)_2$ into hexadecimal.

Solution:

Given Binary number	010	1111	1011	.	0111	11
Group of 4 bits are	= 0010	1111	1011	.	0111	1100
Convert each group into octal =	2	F	B	.	7	C

The result is **$(2FB.7C)_{16}$**

2.DECIMAL NUMBER SYSTEM:-

(a) Decimal to binary conversion:- In the conversion the integer number are converted to the desired base using successive division by the base or radix.

For example: (i) Convert $(52)_{10}$ into binary.

(ii) Convert $(105.15)_{10}$ into binary.

Solution:

Integer part	Fraction part
$2 \overline{) 105}$	$0.15 \times 2 = 0.30$
$2 \overline{) 52} \quad - 1$	$0.30 \times 2 = 0.60$
$2 \overline{) 26} \quad - 0$	$0.60 \times 2 = 1.20$
$2 \overline{) 13} \quad - 0$	$0.20 \times 2 = 0.40$
$2 \overline{) 6} \quad - 1$	$0.40 \times 2 = 0.80$
$2 \overline{) 3} \quad - 0$	$0.80 \times 2 = 1.60$
$2 \overline{) 1} \quad - 1$	
$0 \quad - 1$	

Result of $(105.15)_{10}$ is **$(1101001.001001)_2$**

(b) Decimal to octal conversion:- To convert the given decimal integer number to octal, successively divide the given number by 8 till the quotient is 0.

(i) Convert $(378.93)_{10}$ into octal.

Solution:

$8 \overline{) 378}$	$0.93 \times 8 = 7.44$
$8 \overline{) 47} \quad - 2$	$0.44 \times 8 = 3.52$
$8 \overline{) 5} \quad - 7$	$0.52 \times 8 = 4.16$
$0 \quad - 5$	$0.16 \times 8 = 1.28$

Result of $(378.93)_{10}$ is $(572.7341)_8$

(c) Decimal to hexadecimal conversion:-

(i) Convert $(2598.675)_{10}$ into hexadecimal.

Solution:

	Remainder	Hex		Hex
	Decimal	Hex		Hex
$16 \overline{) 2598}$			$0.675 \times 16 = 10.8$	A
$16 \overline{) 162} \quad - 6$	6	6	$0.800 \times 16 = 12.8$	C
$16 \overline{) 10} \quad - 2$	2	2	$0.800 \times 16 = 12.8$	C
$0 \quad - 10$	A	A	$0.800 \times 16 = 12.8$	C

Result of $(2598.675)_{10}$ is $(A26.ACCC)_{16}$

3. OCTAL NUMBER SYSTEM:-

(a) Octal to binary conversion:- To convert a given a octal number to binary, replace each octal digit by its 3- bit binary equivalent.

For example:

Convert $(367.52)_8$ into binary.

Solution:

Given Octal number is	3	6	7	.	5	2
Convert each group octal to binary	= 011	110	111	.	101	010

Result of $(367.52)_8$ is $(011110111.101010)_2$

(b) Octal to decimal conversion:- For conversion octal to decimal number, multiply each digit in the octal number by the weight of its position and add all the product terms

For example: -

Convert $(4057.06)_8$ to decimal

Solution:

$$\begin{aligned}
 (4057.06)_8 &= 4 \times 8^3 + 0 \times 8^2 + 5 \times 8^1 + 7 \times 8^0 + 0 \times 8^{-1} + 6 \times 8^{-2} \\
 &= 2048 + 0 + 40 + 7 + 0 + 0.0937 \\
 &= (2095.0937)_{10}
 \end{aligned}$$

Result is $(2095.0937)_{10}$

(c) Octal to hexadecimal conversion:- For conversion of octal to Hexadecimal, first convert the given octal number to binary and then binary number to hexadecimal

(4) HEXADECIMAL NUMBER SYSTEM :- (a)Hexadecimal to binary conversion:- For conversion of hexadecimal to binary, replace hexadecimal digit by its 4 bit binary group

Convert (3A9E.B0D)₁₆ into binary.

Solution:

Given Hexadecimal number is 3 A 9 E . B 0 D
 Convert each hexadecimal = 0011 1010 1001 1110 . 1011 0000 1101
 digit to 4 bit binary

Result of (3A9E.B0D)₁₆ is **(0011101010011110.101100001101)₂**

(b)Hexadecimal to decimal conversion:- For conversion of hexadecimal to decimal, multiply each digit in the hexadecimal number by its position weight and add all those product terms.

Convert (A0F9.0EB)₁₆ to decimal

Solution:

$$\begin{aligned} (A0F9.0EB)_{16} &= (10 \times 16^3) + (0 \times 16^2) + (15 \times 16^1) + (9 \times 16^0) + (0 \times 16^{-1}) + (14 \times 16^{-2}) + (11 \times 16^{-3}) \\ &= 40960 + 0 + 240 + 9 + 0 + 0.0546 + 0.0026 \\ &= (41209.0572)_{10} \end{aligned}$$

Result is **(41209.0572)₁₀**

(c) Hexadecimal to Octal conversion:- For conversion of hexadecimal to octal, first convert the given hexadecimal number to binary and then binary number to octal

Arithmetic Operation-Addition, Subtraction, Multiplication, Division, 1's & 2's complement of Binary numbers& Subtraction using complements method

1. BINARY ADDITION:-

The binary addition rules are as follows

$$0 + 0 = 0; \quad 0 + 1 = 1; \quad 1 + 0 = 1; \quad 1 + 1 = 10, \quad \text{SUM, } 1 + 1 + 1 = 11 \quad \text{SUM}$$

Add (100101)₂ and (1101111)₂.

Solution :-

$$\begin{array}{r} 100101 \\ + 1101111 \\ \hline 10010100 \end{array}$$

Result is **(10010100)₂**

2. BINARY SUBTRACTION:-

The binary subtraction rules are as follows

$0 - 0 = 0$; $1 - 1 = 0$; $1 - 0 = 1$; $0 - 1 = 11$, with a borrow of 1

Subtract $(111.111)_2$ from $(1010.01)_2$.

Solution :-

$$\begin{array}{r} 1010.010 \\ - \underline{111.111} \\ \hline 0010.011 \end{array}$$

Result is $(0010.011)_2$

3. BINARY MULTIPLICATION:-

The binary multiplication rules are as follows

$0 \times 0 = 0$; $1 \times 1 = 1$; $1 \times 0 = 0$; $0 \times 1 = 0$

Multiply $(1101)_2$ by $(110)_2$.

Solution :-

$$\begin{array}{r} 1101 \\ \times \underline{110} \\ \hline 0000 \\ 1101 \\ + \underline{1101} \\ \hline 1001110 \end{array}$$

Result is $(1001110)_2$

4. BINARY DIVISION:-

The binary division is very simple and similar to decimal number system.

So we have only 2 rules $0 \div 1 = 0$ $1 \div 1 = 1$

$$\begin{array}{r} 110 \) \ 101101 \ (\ 111.1 \\ - \underline{110} \\ 1010 \\ \underline{110} \\ 1001 \\ \underline{110} \\ 110 \\ \underline{110} \\ 000 \end{array}$$

Result is $(111.1)_2$

1's COMPLEMENT REPRESENTATION :-

The 1's complement of a binary number is obtained by changing each 0 to 1 and each 1 to 0.

Find $(1100)_2$ 1's complement.

Solution :-

Given	1	1	0	0
1's complement is	0	0	1	1

Result is $(0011)_2$

2's COMPLEMENT REPRESENTATION :-

The 2's complement of a binary number is a binary number which is obtained by adding 1 to the 1's complement of a number.

2's complement = 1's complement + 1

Find $(1010)_2$ 2's complement.

Solution :-

Given	1	0	1	0
1's complement is	0	1	0	1
	+			1
2's complement	0	1	1	0

Result is $(0110)_2$

SIGNED NUMBER :-

In sign – magnitude form, additional bit called the sign bit is placed in front of the number. If the sign bit is 0, the number is positive. If it is a 1, the number is negative.

0	1	0	1	0	0	1	=	+41
↑								
Sign bit								
1	1	0	1	0	0	1	=	-41
↑								
Sign bit								

SUBTRACTION USING COMPLEMENT METHOD :

1's COMPLEMENT:-

In 1's complement subtraction, add the 1's complement of subtrahend to the minuend. If there is a carry out, then the carry is added to the LSB. This is called end around carry. If the MSB is 0, the result is positive. If the MSB is 1, the result is negative and is in its 1's complement form. Then take its 1's complement to get the magnitude in binary.

Subtract $(10000)_2$ from $(11010)_2$ using 1's complement.

Solution:-

$$\begin{array}{r}
 11010 \\
 - 10000 \\
 \hline
 \end{array}
 \Rightarrow
 \begin{array}{r}
 11010 \\
 + \underline{01111} \text{ (1's complement)} \\
 \hline
 \text{Carry} \rightarrow 101001 \\
 + \underline{1} \\
 \hline
 \underline{01010} = +10
 \end{array}
 \begin{array}{r}
 = 26 \\
 = -16 \\
 + 10 \\
 = +10
 \end{array}$$

Result is **+10**

2's COMPLEMENT:-

In 2's complement subtraction, add the 2's complement of subtrahend to the minuend. If there is a carry out, ignore it. If the MSB is 0, the result is positive. If the MSB is 1, the result is negative and is in its 2's complement form. Then take its 2's complement to get the magnitude in binary.

Subtract $(1010100)_2$ from $(1010100)_2$ using 2's complement.

Solution:-

$$\begin{array}{r}
 1010100 \\
 - 1010100 \\
 \hline
 \end{array}
 \Rightarrow
 \begin{array}{r}
 1010100 \\
 + \underline{0101100} \text{ (2's complement)} \\
 \hline
 10000000 \text{ (Ignore the carry)} \\
 = 0 \text{ (result = 0)}
 \end{array}
 \begin{array}{r}
 = 84 \\
 = -84 \\
 \underline{0}
 \end{array}$$

Hence MSB is 0. The answer is positive. So it is $+0000000 = 0$

Digital Code & its application & distinguish between weighted & non-weight Code, Binary codes, excess-3 and Gray codes.

DIGITAL CODES:-

In practice the digital electronics requires to handle data which may be numeric, alphabets and special characters. This requires the conversion of the incoming data into binary format before it can be processed. There is various possible ways of doing this and this process is called encoding. To achieve the reverse of it, we use decoders.

WEIGHTED AND NON-WEIGHTED CODES

There are two types of binary codes

1) **Weighted binary codes** : In weighted codes, for each position (or bit), there is specific weight attached. For example, in binary number, each bit is assigned particular weight 2^n where 'n' is the bit number for $n = 0,1,2,3,4$ the weights are 1,2,4,8,16 respectively. Example :- BCD

2) **Non- weighted binary codes:**

Non-weighted codes are codes which are not assigned with any weight to each digit position, i.e., each digit position within the number is not assigned fixed value. Example:- Excess – 3 (XS -3) code and Gray codes

BINARY CODED DECIMAL (BCD):- BCD is a weighted code. In weighted codes, each successive digit from right to left represents weights equal to some specified value and to get the equivalent decimal number add the products of the weights by the corresponding binary digit. 8421 is the most common because 8421 BCD is the most natural amongst the other possible codes.

BCD ADDITION:-

Addition of BCD (8421) is performed by adding two digits of binary, starting from least significant digit. In case if the result is an illegal code (greater than 9) or if there is a carry out of one then add 0110(6) and add the resulting carry to the next most significant.

Add 679.6 from 536.8 using BCD addition.

Solution:-

6 7 9 . 6	0110 0111 1001 . 0110	(679.6 in BCD)
+ 5 3 6 . 8	=>+ 0101 0011 0110 . 1000	(536.8 in BCD)
1 2 1 6 . 4	1011 1010 1111 . 1110	(All are illegal codes)
	+ 0110 +0110 +0110 .+0110	(Add 0110 to each)
	0001 0010 0001 0110 . 0100	
	1 2 1 6 . 4	(corrected sum = 1216.4)

Result is **1216.4**

BCD SUBTRACTION:-

The BCD subtraction is performed by subtracting the digits of each 4 – bit group of the subtrahend from corresponding 4 – bit group of the minuend in the binary starting from the LSD. If there is no borrow from the next higher group[then no correction is required. If there is a borrow from the next group, then 6 (0110) is subtracted from the difference term of this group.

Subtract 147.8 from 206.7 using 8421 BCD code.

Solution:-

2 0 6 . 7	0010 0000 0110 . 0111	(206.7 in BCD)
- 1 4 7 . 8	=>- 0001 0100 0111 . 1000	(147.8 in BCD)
5 8 . 9	0000 1011 1110 . 1111	(Borrows are present)
	- 0110 -0110 .- 0110	
	0101 1000 . 1001	
	5 8 . 9	(corrected difference = 58.9)

Result is **(58.9)₁₀**

EXCESS THREE(XS-3) CODE:-

The Excess-3 code, also called XS-3, is a non- weighted BCD code. This derives its name from the fact that each binary code word is the corresponding 8421 code word plus 0011(3). It is a sequential code. It is a self complementing code.

Excess-3 code is non-weighted and self complementary code. A self complementary binary codes are always compliment themselves. The complement of a binary number can be obtained from that number by replacing 0's with 1's and 1's with 0's. The sum of binary number and its complement is always equal to decimal 9. In other words, the 1's complement of an excess-3 code is the excess-3 code for the 9's complement of the corresponding decimal number.

For example, the excess-3 code for decimal number 5 is 1000 and 1's complement of 1000 is 0111, which is excess-3 code for decimal number 4, and it is 9's complement of number 5.

ASCII CODE:-

The American Standard Code for Information Interchange (ASCII) pronounced as 'ASKEE' is widely used alphanumeric code. This is basically a 7 bit code. The number of different bit patterns that can be created with 7 bits is $2^7 = 128$, the ASCII can be used to encode both the uppercase and lowercase characters of the alphabet (52 symbols) and some special symbols in addition to the 10 decimal digits. It is used extensively for printers and terminals that interface with small computer systems. The table shown below shows the ASCII groups.

GRAY CODE:-

The gray code is a non-weighted code. It is not a BCD code. It is cyclic code because successive words in this differ in one bit position only i.e it is a unit distance code. Gray code is used in instrumentation and data acquisition systems where linear or angular displacement is measured.

BINARY- TO – GRAY CONVERSION:-

If an n-bit binary number is represented by $B_n B_{n-1} \dots B_1$ and its gray code equivalent by $G_n G_{n-1} \dots G_1$, where B_n and G_n are the MSBs, then gray code bits are obtained from the binary code as follows

$$\begin{aligned} G_n &= B_n \\ G_{n-1} &= B_n \oplus B_{n-1} \\ &\vdots \\ &\vdots \\ G_1 &= B_2 \oplus B_1 \end{aligned}$$

Where the symbol \oplus stands for Exclusive OR (X-OR)

GRAY- TO - BINARY CONVERSION:-

If an n-bit gray number is represented by $G_n G_{n-1} \dots G_1$ and its binary equivalent by $B_n B_{n-1} \dots B_1$, then binary bits are obtained from Gray bits as follows :

$$\begin{aligned} B_n &= G_n \\ B_{n-1} &= B_n \oplus G_{n-1} \\ &\vdots \\ &\vdots \\ B_1 &= B_2 \oplus G_1 \end{aligned}$$

Logic gates: AND, OR, NOT, NAND, NOR, Exclusive-OR, Exclusive-NOR-- Symbol, Function, expression, truth table & timing diagram

LOGIC GATES:-

- Logic gates are the fundamental building blocks of digital systems.
- There are 3 basic types of gates AND, OR and NOT.
- Logic gates are electronic circuits because they are made up of a number of electronic devices and components.
- Inputs and outputs of logic gates can occur only in 2 levels(logic 1, logic 0). These two levels are termed HIGH and LOW, or TRUE and FALSE, or ON and OFF
- *The table which lists all the possible combinations of input variables and the corresponding output of any logic circuit/device, called a **truth table**.*


DIFFERENT TYPES OF LOGIC GATES

NOT GATE (INVERTER):-

- A NOT gate, also called an inverter, has only one input and one output.
- It is a device whose output is always the complement of its input.
- The output of a NOT gate is the logic 1 state when its input is in logic 0 state and the logic 0 state when its input is in logic 1 state.

IC No. :- 7404

Logic Symbol

 

Truth table

INPUT A	OUTPUT A
0	1
1	0

AND GATE:-

- An AND gate has two or more inputs but only one output.
- The output is logic 1 state only when each one of its inputs is at logic 1 state.
- The output is logic 0 state even if one of its inputs is at logic 0 state.

IC No.:- 7408

Logic Symbol



Truth Table

		OUTPUT
A	B	Q=A . B
0	0	0
0	1	0
1	0	0
1	1	1

OR GATE:-

- An OR gate may have two or more inputs but only one output.
- The output is logic 1 state, even if one of its inputs is 1
- The output is logic 0 state, only when each one of its inputs is in logic state.

IC No.:- 7432
Logic Symbol



Truth Table

INPUT		OUTPUT
A	B	$Q = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

NAND GATE:-

- NAND gate is a combination of an AND gate and a NOT gate.
- The output is logic 0 when each of the input is logic 1 and for any other combination of inputs, the output is logic 1.

IC No.:- 7400 two input NAND gate

Logic Symbol



Truth Table


INPUT		OUTPUT
A	B	$Q = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

NOR GATE:-

- NOR gate is a combination of an OR gate and a NOT gate.
- The output is logic 1, only when each one of its input is logic 0 and for any other combination of inputs the output is a logic 0 level.

IC No.:- 7402 two input NOR gate

Logic Symbol

 

Truth Table


INPUT		OUTPUT
A	B	$Q = \overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

EXCLUSIVE – OR (X-OR) GATE

- An X-OR gate is a two input, one output logic circuit.
- The output is logic 1 when one and only one of its two inputs is logic 1. When both the inputs is logic 0 or when both the inputs is logic 1, the output is logic 0.

IC No.:- 7486

Logic Symbol

 

INPUTS are A and B

OUTPUT is $Q = A \oplus B$

$$= A\bar{B} + \bar{A}B$$

Truth Table

INPUT		OUTPUT
A	B	$Q = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0


EXCLUSIVE – NOR (X-NOR) GATE

- An X-NOR gate is the combination of an X-OR gate and NOT gate

- An X-NOR gate is a two input, one output logic circuit. The output is logic 1 only when both the inputs are logic 0 or when both the inputs is 1.
- The output is logic 0 when one of the inputs is logic 0 and other is 1

IC No.:- 74266

Logic Symbol

 

$$\begin{aligned} \text{OUT} &= A B + \bar{A} \bar{B} \\ &= A \text{ XNOR } B \end{aligned}$$

INPUT		OUTPUT
A	B	OUT = A XNOR B
0	0	1
0	1	0
1	0	0
1	1	1

Universal Gates & its Realisation


UNIVERSAL GATES:-

There are 3 basic gates AND, OR and NOT, there are two universal gates NAND and NOR. Both NAND and NOR gates can perform all logic functions i.e. AND, OR, NOT, EXOR and EXNOR.

NAND GATE:-

 
a) Inverter from NAND gate

$$\begin{aligned} \text{Input} &= A \\ \text{Output } Q &= \bar{A} \end{aligned}$$



 
b) AND gate from NAND gate

$$\begin{aligned} \text{Input s are } &A \text{ and } B \\ \text{Output } Q &= A.B \end{aligned}$$



 
c) OR gate from NAND gate

$$\begin{aligned} \text{Inputs are } &A \text{ and } B \\ \text{Output } Q &= A+B \end{aligned}$$



 
d) NOR gate from NAND gate

$$\begin{aligned} \text{Inputs are } &A \text{ and } B \\ \text{Output } Q &= \overline{A+B} \end{aligned}$$



 e) **EX-OR gate from NAND gate**


Inputs are **A** and **B**
Output **Q = A B + A B**



 e) **EX-OR** f) **EX-NOR gate From NAND gate**

Inputs are **A** and **B**
Output **C**

Inputs are **A** and **B**
Output **Q = A B + A B**



NOR GATE:-


a) **Inverter from NOR gate**

Input = **A**
Output **Q = A**



 
b) **AND gate from NOR gate**

Inputs are **A** and **B**
Output **Q = A.B**



 
c) **OR gate from NOR gate**

Inputs are **A** and **B**
Output **Q = A+B**



 
d) **NAND gate from NOR gate**

Inputs are **A** and **B**
Output **Q = A.B**



 
e) **EX-OR gate from NOR gate**

Inputs are **A** and **B**
Output **Q = A B + AB**



 
e) **EX-OR gate from NOR gate**

Inputs are **A** and **B**
Output **Q = A B + AB**



 f) **EX-NOR gate From NOR gate**

Inputs are **A** and **B**
Output **Q = A B + A B**



Boolean algebra, Boolean expressions, Demorgan's Theorems.

BOOLEAN ALGEBRA INTRODUCTION:-

- Switching circuits are also called logic circuits, gates circuits and digital circuits.

- Boolean algebra is a system of mathematical logic. It is an algebraic system consisting of the set of elements (0,1), two binary operators called OR and AND and unary operator called NOT.
- It is the basic mathematical tool in the analysis and synthesis of switching circuits.
- It is a way to express logic functions algebraically.

AXIOMS AND LAWS OF BOOLEAN ALGEBRA:-

Axioms or postulates of Boolean algebra are set of logical expressions that are accepted without proof and upon which we can build a set of useful theorems.

Axiom 1: $0 \cdot 0 = 0$ Axiom 5: $0 + 0 = 0$ Axiom 9: $\overline{\overline{1}} = 0$
 Axiom 2: $0 \cdot 1 = 0$ Axiom 6: $0 + 1 = 1$ Axiom 10: $\overline{\overline{0}} = 1$
 Axiom 3: $1 \cdot 0 = 0$ Axiom 7: $1 + 0 = 1$
 Axiom 4: $1 \cdot 1 = 1$ Axiom 8: $1 + 1 = 1$

1. Complementation Laws:-

The term complement simply means to invert, i.e. to changes 0s to 1s and 1s to 0s.

The five laws of complementation are as follows:

- Law 1: $\overline{\overline{0}} = 1$
 Law 2: $\overline{\overline{1}} = 0$
 Law 3: if $A = 0$, then $\overline{A} = 1$
 Law 4: if $A = 1$, then $\overline{A} = 0$
 Law 5: $\overline{\overline{A}} = A$ (double complementation law)

2. OR Laws:-

The four OR laws are as follows

- Law 1: $A + 0 = A$ (Null law)
 Law 2: $A + 1 = 1$ (Identity law)
 Law 3: $A + A = A$
 Law 4: $A + \overline{A} = 1$

3. AND Laws:-

The four AND laws are as follows

- Law 1: $A \cdot 0 = 0$ (Null law)
 Law 2: $A \cdot 1 = A$ (Identity law)
 Law 3: $A \cdot A = A$
 Law 4: $A \cdot \overline{A} = 0$

4. Commutative Laws:-

Commutative laws allow change in position of AND or OR variables. There are two commutative laws.

- Law 1: $A + B = B + A$
 Law 2: $A \cdot B = B \cdot A$

5. Associative Laws:-

The associative laws allow grouping of variables. There are 2 associative laws.

- Law 1: $(A + B) + C = A + (B + C)$
 Law 2: $(A \cdot B) \cdot C = A \cdot (B \cdot C)$

6. Distributive Laws:-

The distributive laws allow factoring or multiplying out of expressions. There are two distributive laws.

$$\text{Law 1: } A(B + C) = AB + AC$$

$$\text{Law 2: } A + BC = (A+B)(A+C)$$

Proof:

$$\text{RHS} = (A+B)(A+C) = AA + AC + BA + BC$$

$$= A + AC + AB + BC$$

$$= A(1 + C + B) + BC$$

$$= A \cdot 1 + BC \quad (1 + C + B = 1 + B = 1, \text{ FROM OR Law 2})$$

$$= A + BC = \text{LHS}$$

7. Redundant Literal Rule (RLR):-

$$\text{Law 1: } A + \bar{A}B = A + B$$

Proof

$$A + \bar{A}B = (A + \bar{A})(A + B)$$

$$= 1 \cdot (A + B)$$

$$= A + B$$

$$\text{Law 2: } A(\bar{A} + B) = AB$$

Proof

$$A(\bar{A} + B) = A\bar{A} + AB = 0 + AB = AB$$

8. Idempotence Laws:-

Idempotence means same value.

$$\text{Law 1: } A \cdot A = A$$

$$\text{Law 2: } A + A = A$$

9. Absorption Laws:-

There are two laws:

$$\text{Law 1: } A + A \cdot B = A$$

$$\begin{aligned} \text{Proof: } A + A \cdot B &= A(1 + B) \\ &= A \cdot 1 = A \end{aligned}$$

$$\text{Law 2: } A(A + B) = A$$

$$\begin{aligned} \text{Proof: } A(A + B) &= A \cdot A + A \cdot B \\ &= A + AB \\ &= A(1 + B) \\ &= A \cdot 1 = A \end{aligned}$$

12. De Morgan's Theorem:-

De Morgan's theorem represents two laws in Boolean algebra.

This law states that the complement of a sum of variables is equal to the product of their individual complements.

$$\text{Law 1: } \overline{A + B} = \bar{A} \cdot \bar{B}$$

Proof

A	B	A + B	$\overline{A + B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

=

A	B	\overline{A}	\overline{B}	$\overline{A} \overline{B}$
0	0	1	1	1
0	1	1	0	0
1	0	0	1	0
1	1	0	0	0

Law 2: $\overline{A \cdot B} = \overline{A} + \overline{B}$

This law states that the complement of a product of variables is equal to the sum of their individual complements.

Proof

A	B	A . B	$\overline{A \cdot B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

=

A	B	\overline{A}	\overline{B}	$\overline{A} + \overline{B}$
0	0	1	1	1
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0

1.1 Represent Logic Expression: SOP & POS forms

SUM - OF - PRODUCTS FORM:-

- This is also called disjunctive Canonical Form (DCF) or Expanded Sum of Products Form or Canonical Sum of Products Form.
- In this form, the function is the sum of a number of products terms where each product term contains all variables of the function either in complemented or uncomplemented form.

The or product term which contains all the variables of the functions either in complemented uncomplemented form is called a **minterm**.

- The minterm is denoted as $m_0, m_1, m_2 \dots$. An 'n' variable function can have 2^n minterms.

$$f(A, B, C) = \sum m(1, 2, 3, 5)$$

PRODUCT- OF - SUMS FORM:-

- This form is also called as Conjunctive Canonical Form (CCF) or Expanded Product - of - Sums
- This is by considering the combinations for which $f = 0$
- Each term is a sum of all the variables.

The sum term which contains each of the 'n' variables in either complemented or uncomplemented form is called a **maxterm**.

- Maxterm is represented as M_0, M_1, M_2, \dots

$$f(A, B, C) = \prod M(0, 4, 6, 7)$$

Karnaugh map (3 & 4 Variables) & Minimization of logical expressions, don't care conditions

KARNAUGH MAP OR K- MAP:-

- The K- map is a chart or a graph, composed of an arrangement of adjacent cells, each representing a particular combination of variables in sum or product form
- The K- map is systematic method of simplifying the Boolean expression.

Mapping of SOP Expression:-

- The n variable K-map has 2^n squares. These squares are called cells.
- A '1' is placed in any square indicates that corresponding minterm is included in the output expression, and a 0 or no entry in any square indicates that the corresponding minterm does not appear in the expression for output.

Unit-2: Combinational logic circuits

COMBINATIONAL LOGIC CIRCUIT

- A combinational circuit consists of logic gates whose outputs at any time are determined from only the present combination of inputs.
- A combinational circuit performs an operation that can be specified logically by a set of Boolean functions. It consists of an interconnection of logic gates. Combinational logic gates react to the values of the signals at their inputs and produce the value of the output signal, transforming binary information from the given input data to a required output data.



Half adder

The most basic arithmetic operation is the addition of two binary digits. This simple addition consists of four possible elementary operations: $0 + 0 = 0$, $0 + 1 = 1$, $1 + 0 = 1$, and $1 + 1 = 10$.

The first three operations produce a sum of one digit, but when both augend and addend bits are equal to 1; the binary sum consists of two digits. The higher significant bit of this result is called a carry.


When the augend and addend numbers contain more significant digits, the carry obtained from the addition of two bits is added to the next higher order pair of significant bits.

A combinational circuit that performs the addition of two bits is called a half adder.

- This circuit needs two binary inputs and two binary outputs.

The input variables designate the augend and addend bits; the output variables produce the sum and carry. Symbols x and y are assigned to the two inputs and S (for sum) and C (for carry) to the outputs. The truth table for the half adder is listed in the below table.


Input		Output	
A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

- The C output is 1 only when both inputs are 1. The S output represents the least significant bit of the sum.
- The simplified Boolean functions for the two outputs can be obtained directly from the truth table.

The simplified sum-of-products expressions are $S = A'B + AB'$ $C = AB$

 - The logic diagram of the half adder implemented in sum of products is shown in the below figure. It can be also implemented with an exclusive-OR and an AND gate.



Full adder

One that performs the addition of three bits (two significant bits and a previous carry) is a full adder. The names of the circuits stem from the fact that two half adders can be employed to implement a full adder.

- A full adder is a combinational circuit that forms the arithmetic sum of three bits.
- It consists of three inputs and two outputs. Two of the input variables, denoted by x and y, represent the two significant bits to be added. The third input, z, represents the carry from

the previous lower significant position. The two outputs are designated by the symbols S for sum and C for carry. The simplified expressions are


$$S = x'y'z + x'yz' + xy'z' + xyz$$

$$C = xy + xz + yz$$


- The logic diagram for the full adder implemented in sum-of-products form is shown in figure

<i>x</i>	<i>y</i>	<i>z</i>	<i>C</i>	<i>S</i>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


Truth Table

 

K-Map for full adder

 

 It can also be implemented with two half adders and one OR gate as shown in the figure.



Half Subtractor


This circuit needs two binary inputs and two binary outputs. The subtraction operation is done by using the following rules as: $0 - 0 = 0$; $0 - 1 = 1$ with borrow 1; $1 - 0 = 1$; $1 - 1 = 0$

Symbols x and y are assigned to the two inputs and D (for difference) and B (for borrow) to the outputs. • The truth table for the half subtractor is listed in the below table

x	y	D	B
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0



The simplified Boolean functions for the two outputs can be obtained directly from the truth table. The simplified sum-of-products expressions are $D = x'y + xy'$ and $B = x'y$

 The logic diagram of the half adder implemented in sum of products is shown in the figure. It can be also implemented with an exclusive-OR and an AND gate with one inverted input.



Full Subtractor

  A full subtractor is a combinational circuit that forms the arithmetic subtraction operation of three bits. It consists of three inputs and two outputs. Two of the input variables, denoted by x and y , represent the two significant bits to be subtracted. The third input, z , is subtracted from the result of the first subtraction.




The binary variable D gives the value of the least significant bit of the difference. The binary variable B gives the output borrow formed during the subtraction process.

Parallel Binary 4 bit adder

A binary adder is a digital circuit that produces the arithmetic sum of two binary numbers.

It can be constructed with full adders connected in cascade, with the output carry from each full adder connected to the input carry of the next full adder in the chain.

 Addition of n -bit numbers requires a chain of n full adders or a chain of one-half adder and $n-1$ full adders. The interconnection of four full-adder (FA) circuits to provide a four-bit binary ripple carry adder is shown in the figure.




The augend bits of A and the addend bits of B are designated by subscript numbers from right to left, with subscript 0 denoting the least significant bit. The carries are connected in a chain through the full adders. The input carry to the adder is C_0 , and it ripples through the full adders to the output carry C_4 . The S outputs generate the required sum bits.

Multiplexer (4:1)

A multiplexer is a combinational circuit that selects binary information from one of many input lines and directs it to a single output line.

 - The selection of a particular input line is controlled by a set of selection lines. Normally, there are 2^n input lines and n selection lines whose bit combinations determine which input is selected. A four-to-one-line multiplexer is shown in the below figure.




Each of the four inputs, I_0 through I_3 , is applied to one input of an AND gate. Selection lines S_1 and S_0 are decoded to select a particular AND gate. The outputs of the AND gates are applied to a single OR gate that provides the one-line output.

- A multiplexer is also called a **data selector**, since it selects one of many inputs and steers the binary information to the output line.

De- multiplexer (1:4)

 The data distributor, known more commonly as a Demultiplexer or “Demux” for short, is the exact opposite of the Multiplexer. • The demultiplexer takes one single input data line and then switches it to any one of a number of individual output lines one at a time. The demultiplexer converts a serial data signal at the input to a parallel data at its output lines as shown below.



The function of the demultiplexer is to switch one common data input line to any one of the 4 output data lines A to D in our example above. As with the multiplexer the individual solid state switches are selected by the binary input address code on the output select pins “a” and “b” as shown

Decoder

A decoder is a combinational circuit that converts binary information from n input lines to a maximum of 2^n unique output lines.

- The decoders presented here are called n -to- m -line decoders, where $m \leq 2^n$. Their purpose is to generate the 2^n (or fewer) minterms of n input variables. Each combination of inputs will assert a unique output. The name decoder is also used in conjunction with other code converters, such as a BCD-to-seven-segment decoder.

A two-to-four-line decoder with an enable input constructed with NAND gates is shown in Fig. • The circuit operates with complemented outputs and a complement enable input. The decoder is enabled when E is equal to 0 (i.e., active-low enable). As indicated by the truth table, only one output can be equal to 0 at any given time; all other outputs are equal to 1. • The output whose value is equal to 0 represents the minterm selected by inputs A and B . • The circuit is disabled when E is equal to 1, regardless of the values of the other two inputs. • When the circuit is disabled, none of the outputs are equal to 0 and none of the minterms are selected.

Unit-3: Sequential logic Circuits


SEQUENTIAL LOGIC CIRCUIT SEQUENTIAL CIRCUIT:

- It is a circuit whose output depends upon the present input, previous output and the sequence in which the inputs are applied.

HOW THE SEQUENTIAL CIRCUIT IS DIFFERENT FROM COMBINATIONAL CIRCUIT?

In combinational circuit output depends upon present input at any instant of time and do not use memory. Hence previous input does not have any effect on the circuit. But sequential circuit has memory and depends upon present input and previous output.

 Sequential circuits are slower than combinational circuits and these sequential circuits are harder to design.



TYPES:-

Sequential logic circuits (SLC) are classified as (i) Synchronous SLC (ii) Asynchronous SLC

- The SLC that are controlled by clock are called synchronous SLC and those which are not controlled by a clock are asynchronous SLC.

- **Clock**:- A recurring pulse is called a clock.

FLIP-FLOP AND LATCH:-

- A flip-flop or latch is a circuit that has two stable states and can be used to store information.

- A flip-flop is a binary storage device capable of storing one bit of information. In a stable state, the output of a flip-flop is either 0 or 1.

- Latch is a non-clocked flip-flop and it is the building block for the flip-flop.

- A storage element in digital circuit can maintain a binary state indefinitely until directed by an input signal to switch state.

- Storage element that operate with signal level are called latches and those operate with clock transition are called as flip-flops. SEQUENTIAL LOGIC CIRCUIT MEMORY

- The circuit can be made to change state by signals applied to one or more control inputs and will have one or two outputs.

- A flip-flop is called so because its output either flips or flops meaning to switch back and forth.

- A flip-flop is also called a bi-stable multi-vibrator as it has two stable states. The input signals which command the flip-flop to change state are called excitations.

- Flip-flops are storage devices and can store 1 or 0.

- Flip-flops using the clock signal are called clocked flip-flops. Control signals are effective only if they are applied in synchronization with the clock signal.

- Clock-signals may be positive-edge triggered or negative-edge triggered.

- Positive-edge triggered flip-flops are those in which state transitions take place only at positive- going edge of the clock pulse.



Types of flip-flops include

a) SR (set-reset) F-F

b) D (data or delay) F-F


c) T (toggle) F-F and

d) JK F-F


SR latch using NOR gate:-

The SR latch is a circuit with two cross-coupled NOR gates or two cross-coupled NAND gates.

 - It has two outputs labeled Q and Q'. Two inputs are there labeled S for set and R for reset.
- The latch has two useful states. When Q=0 and Q'=1 the condition is called reset state and when Q=1 and Q'=0 the condition is called set state. • Normally Q and Q' are complement of each other



SR latch using NAND gate:-

 


Input		Output		Comment
S	R	Q	Q _{Next}	
0	0	0	0	No change
0	0	1	1	
0	1	0	0	Reset
0	1	1	0	
1	0	0	1	Set
1	0	1	1	
1	1	0	X	Prohibited state
1	1	1	X	

Racing Condition:-

In case of a SR latch when S=R=1 input is given both the output will try to become 0. This is called Racing condition.

D LATCH:-

 

Unit-4: Registers, Memories & PLD


Shift Registers-Serial in Serial -out, Serial- in Parallel-out, Parallel in serial out and Parallel in parallel out

REGISTERS INTRODUCTION:-

- The sequential circuits known as register, are used for storage and transfer of binary information in a digital system.
- A register has no characteristics internal sequence of states.
- The storage capacity of a register is defined as the number of bits of digital data, it can store or retain.

SERIAL IN, SERIAL OUT SHIFT REGISTER:-

 - This type of shift register accepts data serially, i.e., one bit at a time and also outputs data serially.
- The logic diagram of a four bit serial in, serial out shift register is shown in below figure:




- In 4 stages i.e. with 4 FFs, the register can store upto 4 bits of data.
- Serial data is applied at the D input of the first FF. The Q output of the first FF is connected to the D input of the second FF, the output of the second FF is connected to the D input of the third FF and the Q output of the third FF is connected to the D input of the fourth FF.

The data is outputted from the Q terminal of the last FF.

- When a serial data is transferred to a register, each new bit is clocked into the first FF at the positive going edge of each clock pulse.
- The bit that is previously stored by the first FF is transferred to the second FF. • The bit that is stored by the second FF is transferred to the third FF, and so on.
- The bit that was stored by the last FF is shifted out.


SERIAL IN, PARALLEL OUT SHIFT REGISTER:-

- In this type of register, the data bits are entered into the register serially, the data stored in the register serially, but the stored in the register is shifted out in the parallel form.
- When the data bits are stored once, each bits appears on its respective output line and all bits are available simultaneously.
- The logic diagram and logic symbol of a 4 bit serial in, parallel out shift register is given below.

 

PARALLEL IN, SERIAL OUT SHIFT REGISTER:-

 - For parallel in, serial out shift register the data bits are entered simultaneously into their respective stages on parallel lines, but the data bits are transferred out of the register serially, i.e., on a bit by bit basis over a single line.
- The logic diagram and logic symbol of 4 bit parallel in, serial out shift register using D FFs is shown below.




- There are four data lines A, B, C and D through which the data is entered into the register in parallel form.
- The signal Shift /LOAD allows 1. The data to be entered in parallel form into the register and 2. The data to be shifted out serially from terminal Q4.
 - When Shift /LOAD line is HIGH, gates G1, G2, and G3 are disabled, but gates G4, G5 and G6 are enabled allowing the data bits to shift right from one stage to next.
 - When Shift /LOAD line is LOW, gates G4, G5 and G6 are disabled, whereas gates G1, G2 and G3 are enabled allowing the data input to appear at the D inputs of the respective FFs.

- When clock pulse is applied, these data bits are shifted to the Q output terminals of the FFs and therefore the data is inputted in one step.
- The OR gate allows either the normal shifting operation or the parallel data entry depending on which AND gates are enabled by the level on the Shift /LOAD input.

PARALLEL IN, PARALLEL OUT SHIFT REGISTER:-

 - In a parallel in, parallel out shift register, the data entered into the register in parallel form and also the data taken out of the register in parallel form. Immediately following the simultaneous entry of all data bits appear on the parallel outputs.
- The figure shown below is a 4 bit parallel in parallel out shift register using D FFs.



Logic diagram of a 4 – bit parallel in, parallel out shift register

- Data applied to the D input terminals of the FFs.
- When a clock pulse is applied at the positive edge of that pulse, the D inputs are shifted into the Q outputs of the FFs.
- The register now stores the data. The stored data is available instantaneously for shifting out in parallel form.

APPLICATIONS OF SHIFT REGISTERS

1. Time delays: • In digital systems, it is necessary to delay the transfer of data until it has been completed, or to synchronize the arrival of data at a subsystem where it is processed with other data. • A shift register can be used to delay the arrival of serial data by a specific number of clock pulses, since the number of stages corresponds to the number of clock pulses required to shift each bit completely through the register. • The total time delay can be controlled by adjusting the clock frequency and by the number of stages in the register. • In practice, the clock frequency is fixed and the total delay can be adjusted only by controlling the number of stages through which the data is passed.

2. Serial / Parallel data conversion: • Transfer of data in parallel form is much faster than that in serial. • Similarly the processing of data is much faster when all the data bits are available simultaneously. Thus in digital systems in which speed is important so to operate on data in parallel form is used. • When large data is to be transmitted over long distance, it is costly and impracticable. • It is convenient and economical to transmit data in serial form, since serial data transmission requires only one line.

Unit-5: A/D and D/A Converters

A **Digital to Analog Converter (DAC)** converts a digital input signal into an analog output signal. The digital signal is represented with a binary code, which is a combination of bits 0 and 1.


Types of DACs

There are **two types** of DACs

- Weighted Resistor DAC
- R-2R Ladder DAC

Binary-Weighted Resistor DAC

 A weighted resistor DAC produces an analog output, which is almost equal to the digital (binary) input by using **binary weighted resistors** in the inverting adder circuit. In short, a binary weighted resistor DAC is called as weighted resistor DAC. The **circuit diagram** of a 3-bit binary weighted resistor DAC is shown in the following figure –



The bits of a binary number can have only one of the two values. i.e., either 0 or 1. Let the **3-bit binary input** is $b_2 b_1 b_0$. Here, the bits b_2 and b_0 denote the **Most Significant Bit (MSB) and Least Significant Bit (LSB)** respectively.

The **digital switches** shown in the above figure will be connected to ground, when the corresponding input bits are equal to '0'. Similarly, the digital switches shown in the above figure will be connected to the negative reference voltage, $-V_R$ when the corresponding input bits are equal to '1'.

In the above circuit, the non-inverting input terminal of an op-amp is connected to ground. That means zero volts is applied at the non-inverting input terminal of op-amp. The OP-Amp is performing summation of all currents entering through its inverting terminal.

If the output voltage of the opamp is V_o , then

$$V_o = -I * R_f$$

$$V_o = -(I_0 + I_1 + I_2) * R_f$$

$$\Rightarrow \frac{V_0}{R_f} = \frac{V_R b_2}{2^0 R} + \frac{V_R b_1}{2^1 R} + \frac{V_R b_0}{2^2 R}$$

$$\Rightarrow V_0 = \frac{V_R R_f}{R} \left\{ \frac{b_2}{2^0} + \frac{b_1}{2^1} + \frac{b_0}{2^2} \right\}$$

The **disadvantages** of a binary weighted resistor DAC are as follows –

- The difference between the resistance values corresponding to LSB & MSB will increase as the number of bits present in the digital input increases.
- It is difficult to design more accurate resistors as the number of bits present in the digital input increases.

Successive Approximation A/D Converter:

This is the most widely used A/D converter. The basic principle of this type of A/D converter is that the unknown analog input voltage is approximated against an n-bit digital value by trying one bit at a time, beginning with the MSB. This type of ADC operates by successively dividing the voltage range by half, as explained in the following steps. It consists of a successive approximation register (SAR), DAC and comparator. The output of SAR is given to n-bit DAC. The equivalent analog output voltage of DAC, V_D is applied to the non-inverting input of the comparator. The second input to the comparator is the unknown analog input voltage V_A . The output of the comparator is used to activate the successive approximation logic of SAR.

The configuration of successive approximation process for a 4-bit conversion is explained here. When the start command is applied, the SAR sets the MSB to logic 1 and other bits are made logic 0, so that the trial code becomes 1000

(1) The MSB is initially set to 1 with the remaining three bits set as 000. The digital equivalent voltage is compared with the unknown analog input voltage.

(2) If the analog input voltage is higher than the digital equivalent voltage, the MSB is retained as 1 and the second MSB is set to 1. Otherwise, the MSB is set to 0 and the second MSB is set to 1. Comparison is made as given in step (1) to decide whether to retain or reset the second MSB.

The above steps are more accurately illustrated with the help of an example.


Let us assume that the 4-bit ADC is used and the analog input voltage is $V_A = 11$ V. when the conversion starts, the MSB bit is set to 1.

Now $V_A = 11\text{V} > V_D = 8\text{V} = [1000]_2$

Since the unknown analog input voltage V_A is higher than the equivalent digital voltage

Since the analog input (26.1 V) is less than D/A output (i.e. 32 V) the MSB is set to zero. Then 1 is placed in bit next to MSB. Now the output of D/A is 16 V. Since analog input is more than 16 V, this 1 is retained in this bit position. Next 1 is placed in third bit position.

Now the D/A output is 24 V which is less than analog input. Therefore this 1 bit is retained and 1 is placed in the next bit. Now the D/A output is 28 V, which is more than analog input. Therefore this 1 bit is set to zero and 1 is placed in 5th bit position producing a D/A output of 26 V. It is less than analog input. Therefore this 1 bit is retained. Now 1 is placed in LSB producing a D/A output of 27 V which is more than analog input. Therefore LSB is set to zero and the converter gives an output of 26 V. The successive approximation method of A/D converter is very fast and takes only about 250 ns/ bit

 

Unit-6: LOGIC FAMILIES

A circuit configuration or approach used to produce a type of digital integrated circuit is called Logic Family.

By using logic families we can generate different logic functions, when fabricated in the form of an IC with the same approach, or in other words belonging to the same logic family, will have identical electrical characteristics. The set of digital ICs belonging to the same logic family are electrically compatible with each other.

Some common Characteristics of the Same Logic Family include Supply voltage range, speed of response, power dissipation, input and output logic levels, current sourcing and sinking capability, fanout, noise margin, etc.

TYPES OF LOGIC FAMILY ACCORDING TO IC FABRICATION

- The entire range of digital ICs is fabricated using either bipolar devices or MOS devices or a combination of the two.

Bipolar families include:-

Diode logic (DL)

Resistor-Transistor logic (RTL)

Diode-transistor logic (DTL) Transistor-

Transistor logic (TTL)

Emitter Coupled Logic (ECL), (also known as Current Mode Logic(CML))

Integrated Injection logic (I²L)


The Bi-MOS logic family uses both bipolar and MOS devices.

MOS families include:-

The PMOS family (using P-channel MOSFETs)

The NMOS family (using N-channel MOSFETs)

 The CMOS family (using both N- and P-channel devices)



CHARACTERISTICS OF LOGIC FAMILY:-

DC Supply Voltage:-

- The nominal value of the dc supply voltage for TTL (transistor-transistor logic) and CMOS (complementary metal-oxide semiconductor) devices is +5V. this voltage is connected to V_{cc} or VDD pin of an IC package and ground is connected to the GND pin.

Noise Immunity:-

It is an unwanted signal that is superimposed on the normal operating signal. Noise may be due to various factors like operating environment, radiations, stray electrical and magnetic fields.

In digital logic circuits, the binary values 0 and 1 represent the LOW and HIGH voltage levels. Due to the interference of the noises, the voltage levels may increase or decrease. This may lead to the wrong operation of the device.

- Noise is the unwanted voltage that is induced in electrical circuits and can present a threat to the poor operation of the circuit. In order not to be adversely effected by noise, a logic circuit must have a certain amount of 'noise immunity'. • This is the ability to tolerate a certain amount of unwanted voltage fluctuation on its inputs without changing its output state is called Noise Immunity.

Noise Margin:-

- A measure of a circuit's noise immunity is called 'noise margin' which is expressed in volts.
- There are two values of noise margin specified for a given logic circuit: the HIGH (VNH) and LOW (VNL) noise margins

Power Dissipation :

It is the amount of power that the digital circuit dissipates. The power dissipated is determined by the average current, that is drawn from the supply voltage.

Propagation delay


When a signal passes (propagates) through a logic circuit, it always experiences a time delay. It is the time interval between the application of the input pulse and the occurrence of the output. It is an important characteristic of the digital logic family. If the propagation delay is less, then the **speed** at which the IC operates will be faster.

Fan-in refers to the number of inputs in a digital logic gate family. For the example given in the figure below, the EX-OR gate has three inputs. So fan-in for the given EX-OR gate is 3.



Fan Out of Gates:-

 - When the output of a logic gate is connected to one or more inputs of other gates, a load on the driving gate is created. The maximum number of load gates that a given gate can drive is called the 'Fan-Out' of the gate. For example, the following circuit has an EX-OR gate, which drives 4 NOT gates. So fan-out of EX-OR gate is 4.



Reference

1. Digital logic and computer design by M. Morris Mano.
2. Modern Digital Electronics by RP JAIN TMH
3. Fundamental of Digital Electronics by Ananda Kumar-PHI Publication 3. Digital Electronics by P.RAJA ,SCITECH Publication
4. Digital Electronics by DK Kharate