

**TH4(a) Fundamentals of Electrical & Electronics Engineering**

**Full Marks: 70**

**Time- 3 Hrs**

**Answer any four Questions including Q No.1& 2**  
**Figures in the right hand margin indicates marks**

1. Answer **All** questions 2 x 10
  - a. Define Ohm's law.
  - b. State the difference between periodic and aperiodic signal.
  - c. Write down two characteristics of an ideal op-amp.
  - d. State De-Morgan's theorem.
  - e. Draw the symbols of different types of inductors.
  - f. Define R.M.S value of Alternating Current.
  - g. Write the truth table of a D flip-flop.
  - h. Name the different types of power in A.C circuit & draw the power triangle.
  - i. Write the e.m.f equation of a transformer.
  - j. Draw the symbol of a P-channel FET.
  
2. Answer **Any Six** Questions 5 X 6
  - a. Draw the circuit diagram for both Parallel and Series circuit connection. 2.5+2.5
    - 1) Find the total resistance of the three resistors connected in parallel having the value  $12\Omega$ ,  $4\Omega$  and  $6\Omega$ .
    - 2) Find the total resistance of the three resistors connected in series having the value  $12\Omega$ ,  $4\Omega$  and  $6\Omega$ .
  - b. Explain the working of Light Emitting Diode.
  - c. Describe the analogy between an electric and magnetic circuit.
  - d. With neat diagram explain the working principle of D.C motor.
  - e. A pure resistance of  $50\Omega$  is in series with a pure capacitance of  $100\ \mu\text{F}$ . 1 x 5  
 The series combination is connected across  $100\text{V} - 50\text{ Hz}$  supply.  
 Find a) Impedance, b) Current, c) Power Factor, d) Phase angle, e) Voltage across resistor and capacitor and draw the vector diagram.
  - f. Differentiate between Open Loop and Closed loop configuration of Op-Amp.
  - g. Convert
    - i)  $(10111001)_2$  to Hexadecimal. (1)
    - ii)  $(9BA)_{16}$  to Decimal (1.5)
    - iii)  $(432)_{10}$  to Octal (1.5)
    - iv)  $(10111001)_2$  to Octal. (1)

**Answer any Two Questions.**

3. Define counter. With neat diagram describe the working of Up-down counter. 10
4. Explain the working of Op-Amp as differentiator and integrator. 10
5. Derive the basic equation of different types of DC motor. 10
6. Describe the voltage and current relationship in star delta connection. 10